

## D.C. Motor [Ch-2]

Motor is a electrical device which converts electric energy into mechanical energy.

principle :-

Motor works on a principle that when a current carrying conductor is placed in a magnetic field, it experiences a mechanical force whose direction is given by ~~flemings~~ <sup>left</sup> hand rule and whose magnitude is given by  $F = BIL$  newton,

Back em.f.

$$I_a = \frac{V - E_b}{R_a}$$

Maximum power developed

$$P_m = VI_a - I_a^2 R_a$$

$$\frac{dP_m}{dI_a} = V - 2I_a R_a = 0$$

$$2I_a R_a = \frac{V}{2}$$


$$V = E_b + I_a R_a$$

$$E_b = \frac{V}{2}$$

=
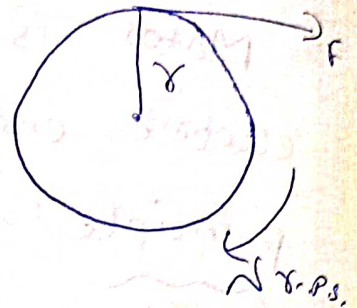
# Torque

Torque is the turning or twisting moment of a force about an axis.



$$T = F \times r$$

Work done for one revolution

$$= \text{force} \times \text{distance}$$

$$= \underline{F \times 2\pi r} \text{ Joule}$$

$$\text{Power developed} = \underline{F \times 2\pi r \times N} \text{ Joule/second}$$

$$= \underline{(F \times r) \times 2\pi N} \text{ watt}$$

$$P = T \times \underline{\omega}$$

$$P = \frac{2\pi N}{60} \times T \text{ watt}$$

$$P = \frac{NT}{9.55} \text{ watt}$$

$$E_b I_a = T_a \times 2\pi N$$

$$E_b = \phi Z N (P/A) V$$

$$T_a \times 2\pi N = \phi Z N (P/A) \times I_a$$

$$T_a = \frac{1}{2\pi} \phi Z I_a (P/A)$$

$$T_a = 0.159 \phi Z I_a (P/A) \text{ N m}$$

$$T_a = \frac{E_b I_a}{2\pi N} = \frac{60 E_b I_a}{2\pi N} = 9.55 \frac{E_b I_a}{N}$$

$N = \underline{\underline{\text{rps}}}$

$$T_{sh} = \frac{\text{output in watt}}{\frac{2\pi N}{60}}$$

$$T_{sh} = 9.55 \frac{\text{output}}{N}$$

Speed of a DC motor

$$E_b = \frac{p \phi N Z}{60 A}$$

$$N = \frac{E_b}{\phi} \times \left( \frac{60 A}{p Z} \right)$$

$$N = K \frac{E_b}{\phi}$$

For series motor

$$\phi \propto I_a$$

So

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{I_{a1}}{I_{a2}}$$

For shunt motor

$$\phi \propto \text{const.}$$

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

Speed Regulation :-

It is the ratio of difference in speed from no load to full load to the full load speed

$$\% \text{ Speed regulation} = \frac{\text{N.L. Speed} - \text{FL Speed}}{\text{FL Speed}} \times 100$$

## Motor characteristics

① Torque and armature current

$$T_a / I_a \text{ (electrical)}$$

② Speed and armature current

$$N / I_a \text{ characteristics}$$


③ Speed and Torque

$$N / T_a \text{ charac.}$$

$$T_a \propto \phi I_a, \quad N \propto \frac{E_b}{\phi}$$


## Characteristics of series motor

$T_a / I_a$  characteristic

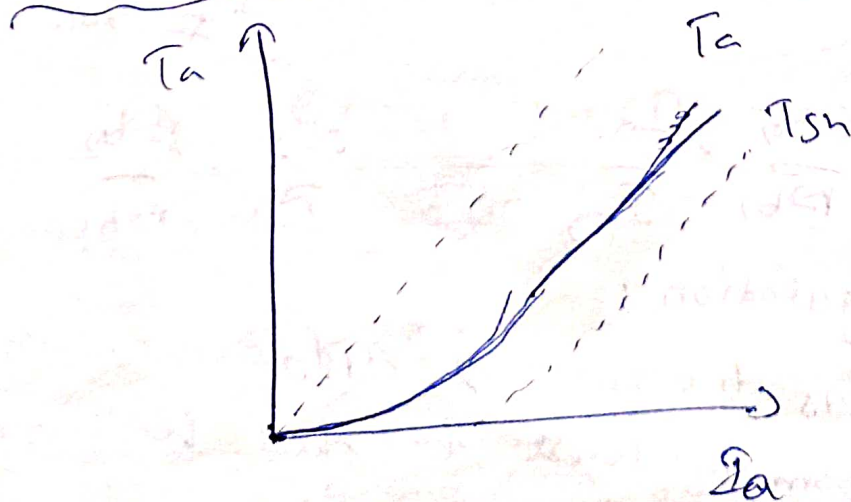

Before magnetic saturation on heavy loads a series motor exerts a torque proportional to the square of armature current. So where huge starting torque is required for accelerating heavy masses quickly as in hoists and electric trains etc.


N/I<sub>a</sub> characteristics

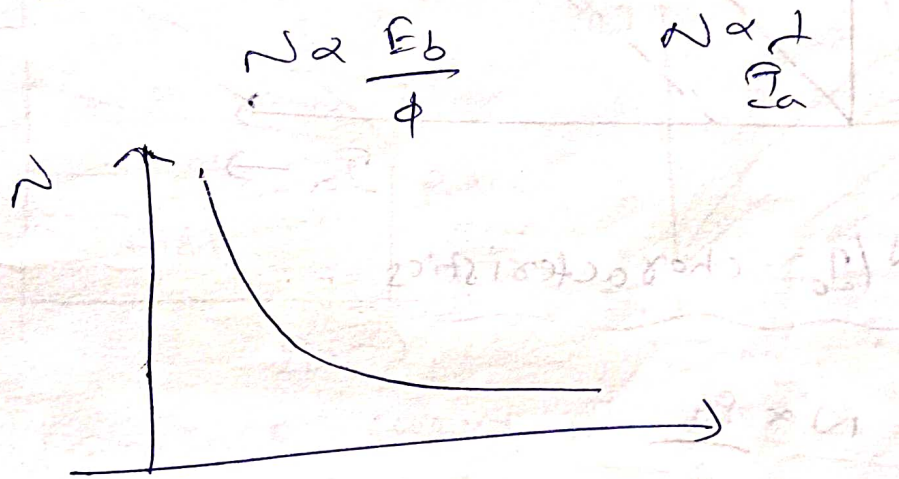

When load current falls to a small value, speed becomes dangerously high.

N/T<sub>a</sub> characteristics :-


From above

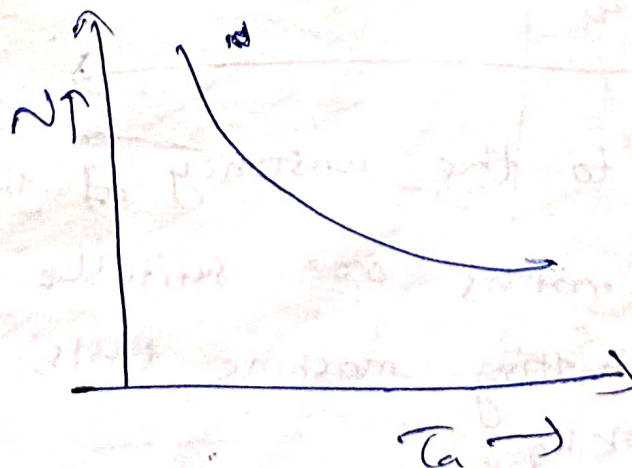

## Characteristics of shunt motor

①  $T_a / I_a$  characteristic

as  $\phi = \text{const.}$

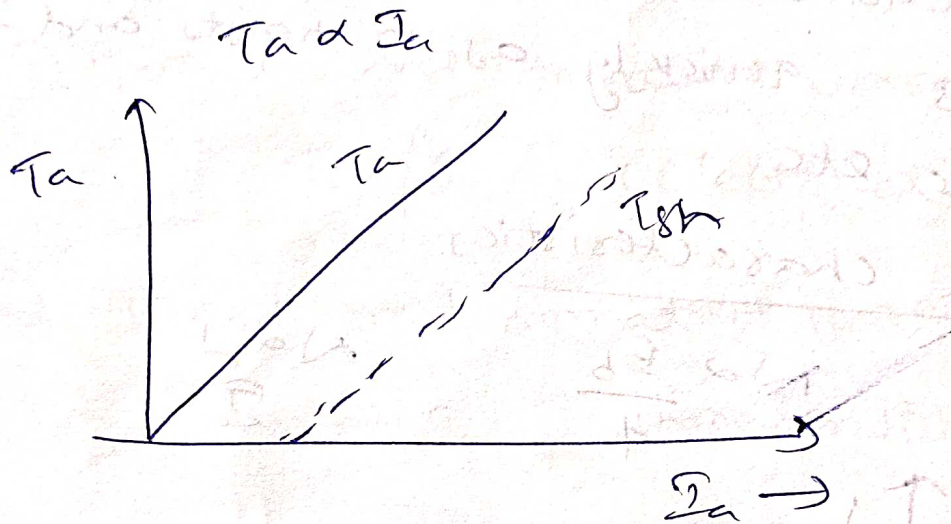


②  $N / I_a$  characteristics

$$N \propto \frac{E_b}{\phi}$$


$\phi = \text{const.}$
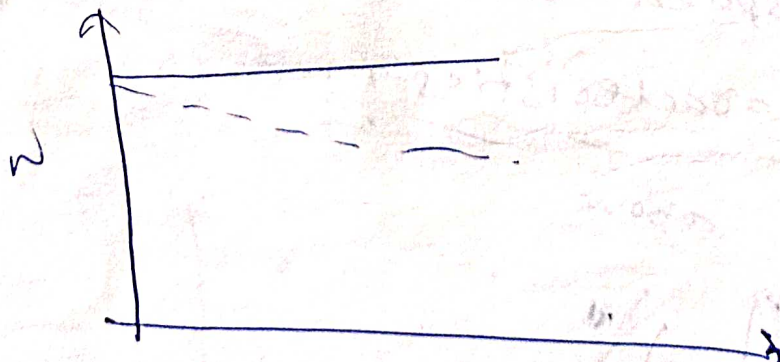
$$N \propto E_b \quad E_b = \text{const.}$$



Due to the constancy of their speed shunt motors are suitable for driving shelling, machine tools, lathes, wood working.

# N/ta characteristics :-


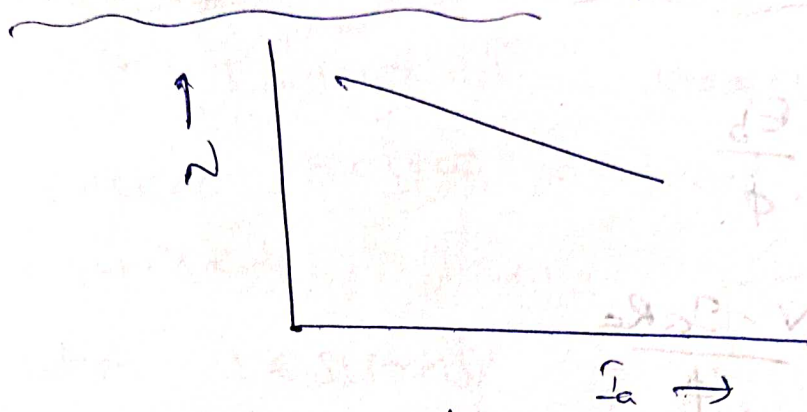


# Compound motors :-


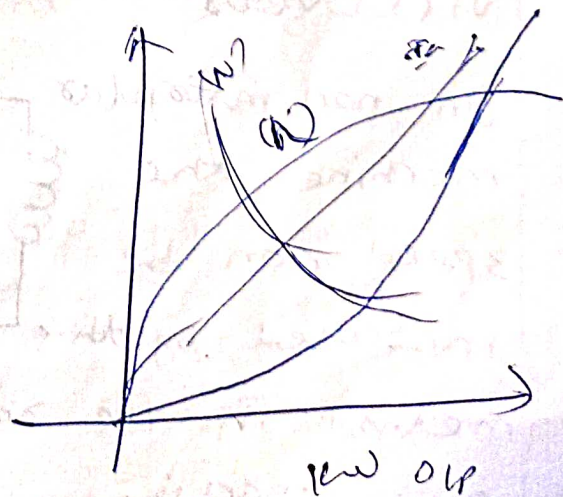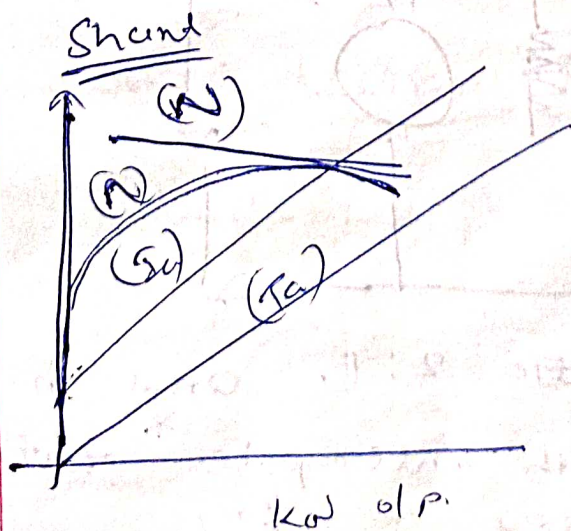
# performance curve of motor

When four essential characteristics i.e. torque, current, speed & efficiency plotted as a function of motor output power known as performance curves of a motor.



# Speed control of DC motors

$$N \propto \frac{E_b}{\phi}$$

$$N \propto \frac{V - I_a R_a}{\phi}$$

Factors controlling speed

→  $\phi$  (flux control)

→  $R_a$  (Resistance  $R_a$ ) (Rheostatic control)

→  $V$  (voltage control)

## Speed control of shunt motors


### Flux control method

$$N \propto \frac{1}{\phi}$$

By decreasing the flux the speed can be increased, and

vice versa.

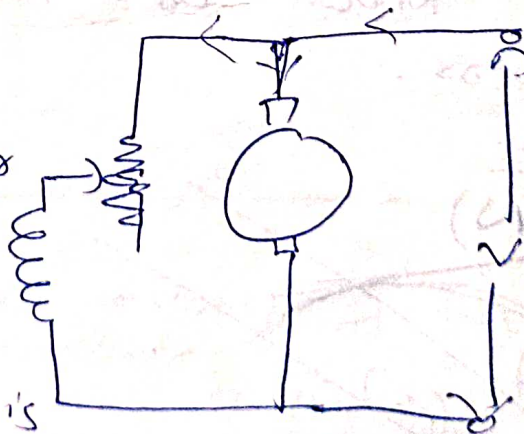In non interpolar machine the speed can be increased by this




method in the ratio 2:1. and in case machine with interpole ratio max to min speed is 6:1


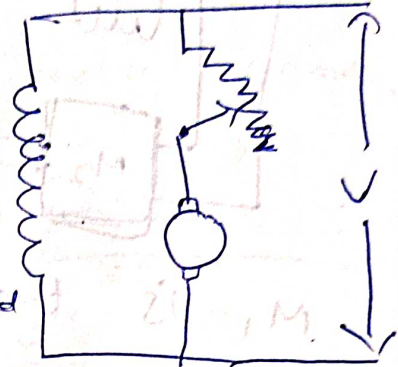
## Armature of Rheostatic control method

This method is ~~used~~ used when speeds below no-load speed are required.

When resistance is increased p.d. across the armature decreased and hence speed decreased.




## Voltage control method

### multiple voltage control

In this method armature is supplied with different voltages by connecting it across one of the several different voltages, by ~~means of~~ the armature voltage is approximately proportional to these different voltages.

## Ward Leonard System

wide range (10:1)

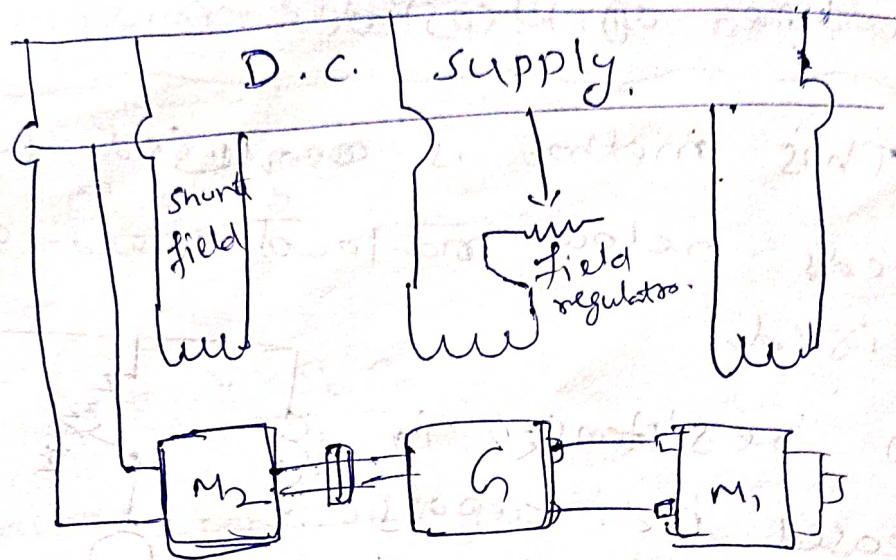

$M_1$  is the main motor whose speed control is required.


The motor  $M_2$  runs at approximately const. speed. The output voltage of G is directly fed to the main motor  $M_1$ . The voltage of the generator can be varied from zero up to its maximum value by means of its field regulator.

## Speed control of DC series motor

### Flux control method
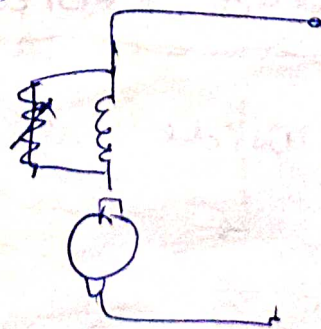
#### (a) field diverters

The series winding shunted by a variable resistance known as



field divertor. Any desired amount of current can be passed through the divertor by adjusting its resistance. Hence the flux can be decreased and consequently speed of motor increased.

(b) Armature divertor :-


$$T \propto \phi I_a$$

When  $I_a$  is reduced

$\phi$  increases

$$\omega \propto \frac{1}{\phi}$$


Speed falls.

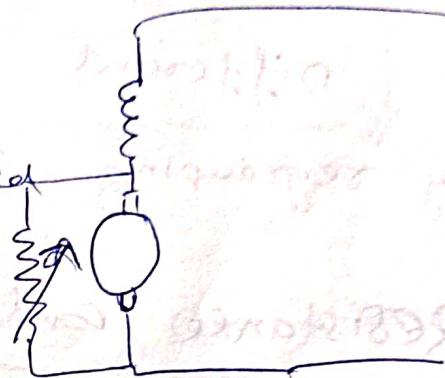


(c) Tapped field control

With full field the motor runs at its minimum speed which can be raised in steps by cutting

some of the series turns.

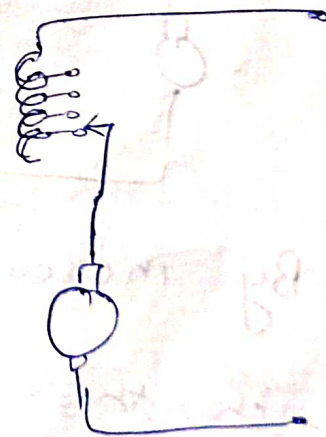


## Paralleling field coils

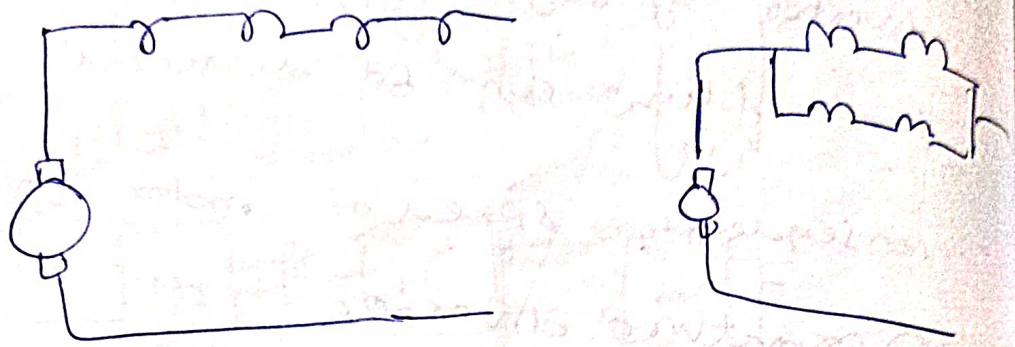

Different speeds can be obtained by regrouping the field coils.

## Resistance control of variable resistance


In series with motor :-

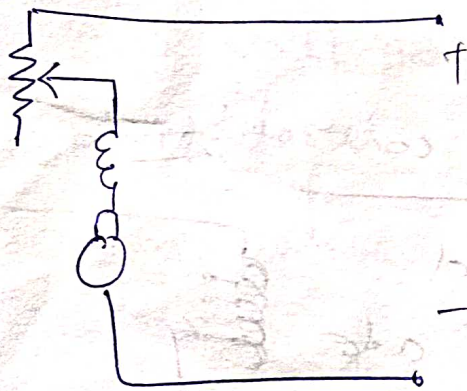

By increasing the resistance in series with the armature the voltage applied across the armature terminals can be decreased, & thus speed is decreased.

there is more power loss in this method.


## Paralleling field coils

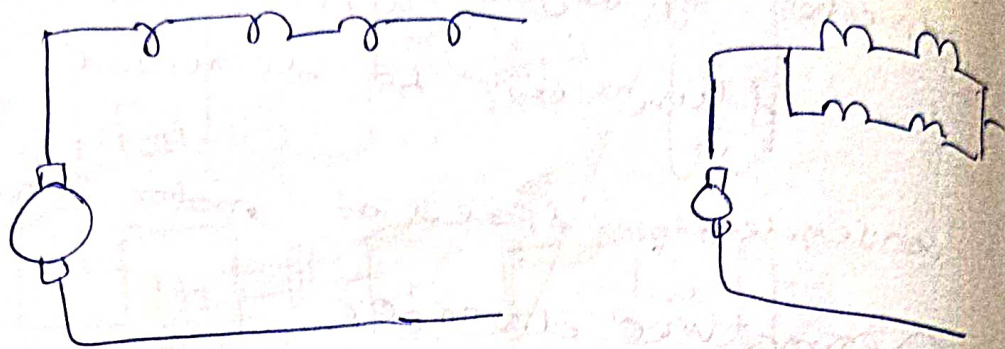

Different speeds can be obtained by regrouping the field coils.

## Resistance control or variable resistance

In series with motor :-

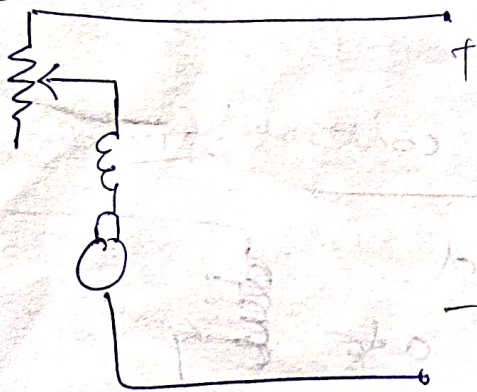


By increasing the resistance in series with the armature the voltage across the armature terminals can be decreased, & thus speed is decreased.

there is more power loss

in this method.

# Series parallel control

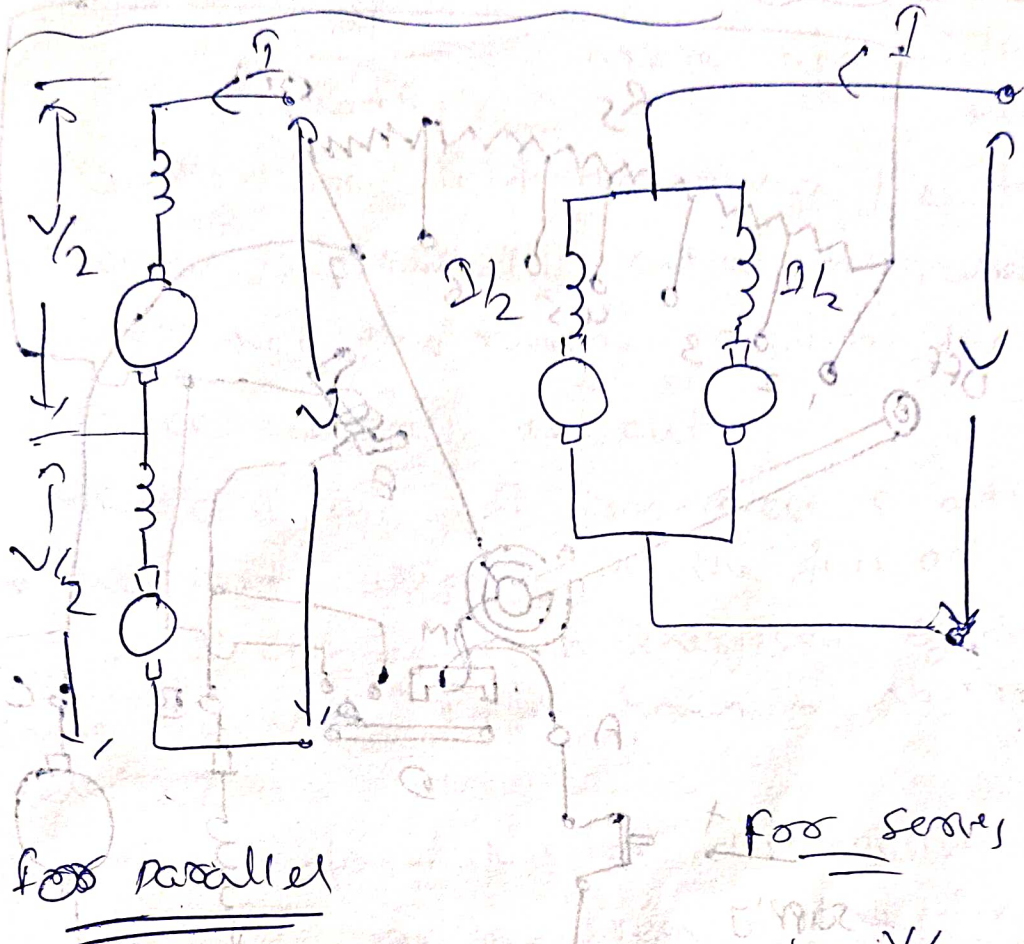

Speed  $\propto \frac{V}{I/2} \propto \frac{2V}{I}$


for series  $N \propto \frac{V/2}{I} \propto \frac{V}{2I}$

in parallel speed is 4 times compared to series.

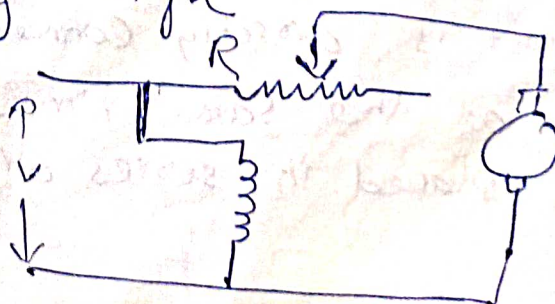
## Necessity of a starter

We know  $I_a = \frac{V - E_b}{R_a}$

At starting as  $N=0$ ,  $E_b=0$ , and  $v$  is full and  $R_a$  is small. So  $I_a$  will be very high



## 3 point starter

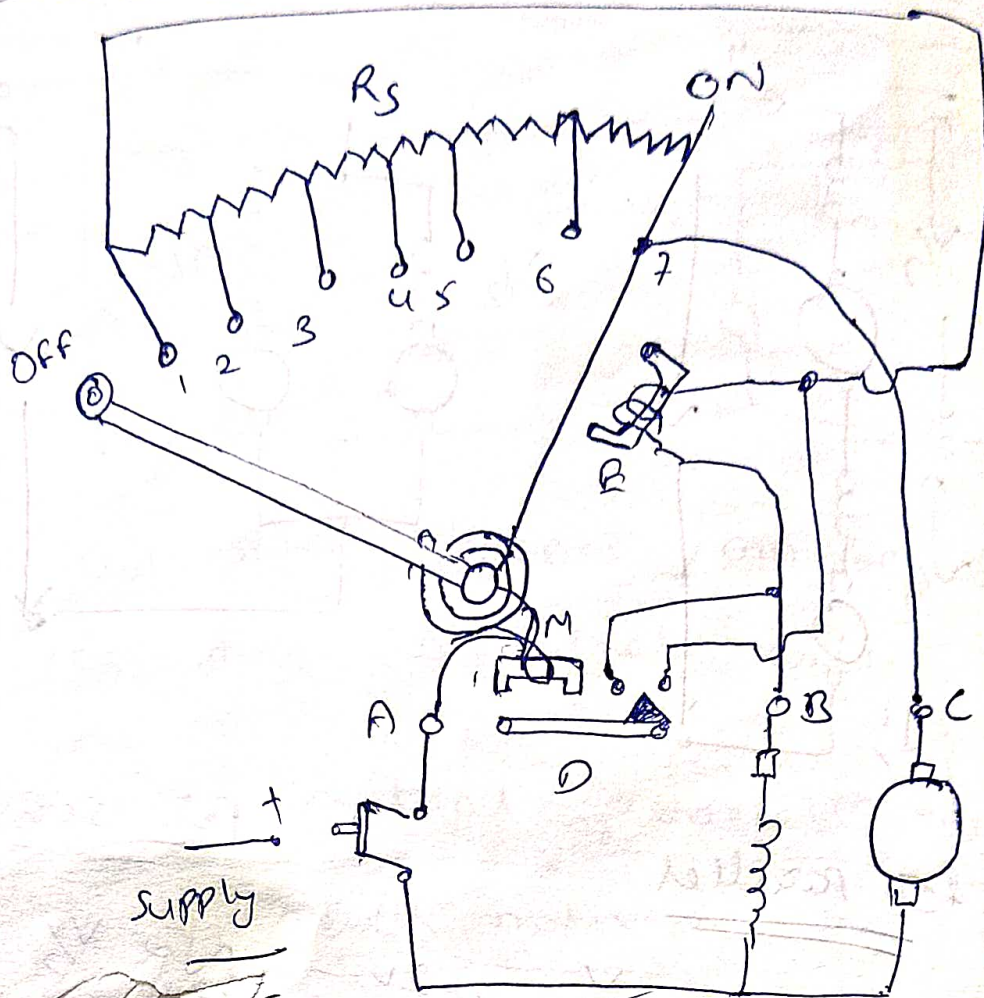

Three terminals A, B, C

C is connected to armature  
B to field & A is connected  
to line through overcurrent release.

To start the motor the main switch is first closed and then the starting arm is slowly moved to the right. As soon as the arm makes contact with stud no. 1 the field circuit is directly connected across the line and at the same time full starting resistance R is placed in series with the armature.

The starting current drawn by armature  
$$= \frac{V}{R_a + R_s}$$
 where  $R_s =$  starting resistance.

As the arm is further moved the starting resistance is gradually cut out till, when the arm reaches the running position, the resistance is all cut out.

There is a soft iron piece  $S$  attached to the arm which is in the full ON held by an electromagnet  $E$  energised by the shunt current. It is known as No-voltage release.

In case of failure or disconnection of the supply ~~or~~ ~~the~~ break in the field circuit ~~is~~ No voltage (Hold on) release is deenergised, there by releasing the arm which is pulled back by the spring to the OFF position.

The overcurrent release consists of an electromagnet connected in the supply line. If the motor becomes overloaded beyond a certain predetermined value, the D is lifted and short circuits the electromagnet. Hence the arm is released and returns to OFF position.




## ~~Advantage~~ Limitation of 3-point starters

If it is desired to control the speed of the motor then field rheostat is connected in the field circuit. The motor speed can be increased by weakening the flux. But if too much resistance is cut in by the field rheostat, then field current is reduced very much so that it is unable to create enough electromagnetic pull to overcome the spring tension, hence arm is pulled ~~back~~ to off position, so it is unsuitable for use with variable speed motors.
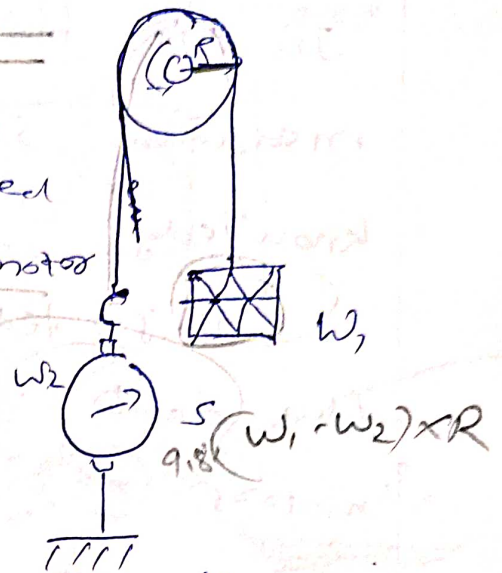
# Brake test

It is a direct method.  
It consists of applying a brake to a water cooled pulley mounted on the motor shaft.

One end of the band is fixed to earth via a spring balance and the other is connected to a suspended weight  $W_1$ .



$W_1$  = Suspended weight in kg.

$W_2$  = Reading of spring balance in kg.

$R$  = Radius of the pulley in metre

$N$  = motor speed in R.P.S.

Shaft torque  $\equiv (W_1 - W_2) \times R$  kg-m

$$T_{sh} = 9.81 (W_1 - W_2) \times R \text{ N-m}$$

Motor output power =  $(T_{sh} \times 2\pi N)$  watt

$$= 2\pi \times 9.81 \text{ N } (W_1 - W_2) R \text{ watt}$$

$$= 61.68 \text{ N } (W_1 - W_2) R \text{ watt}$$


$$\eta = \frac{\text{Output}}{\text{Input}} = \frac{61.68 \text{ N } (W_1 - W_2) R}{V \cdot I}$$

# Swinburne's test (No-load test) (V)

In this method losses are calculated measured separately and from this knowledge efficiency

This test is applicable to const. flux device like shunt and compound motors.

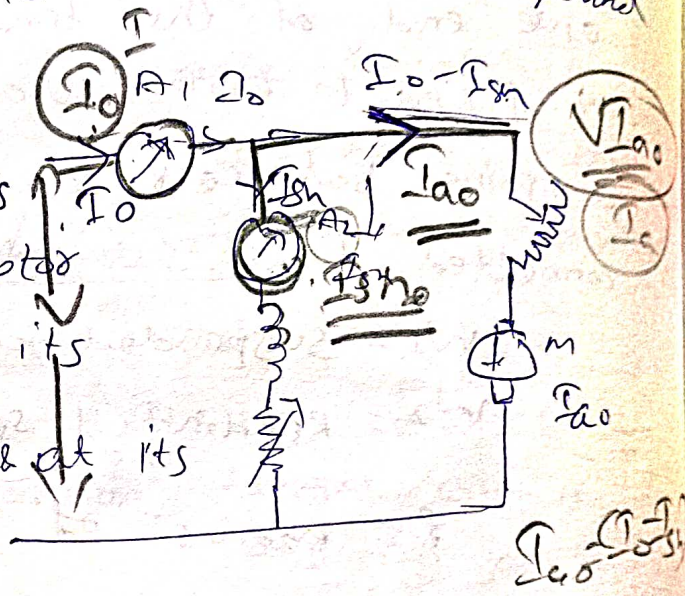The machine is running as a motor on no-load at its rated voltage at its rated speed.



NO-load current by  $A_1 - I_0$

Shunt field current by  $A_2 - I_{sh}$

No load armature current =  $I_0 - I_{sh} = I_{a0}$

Total input =  $V I_0$

power input to armature =  $V I_{a0} = V (I_0 - I_{sh})$

power input to shunt =  $V I_{sh}$

armature power includes

- (i) iron loss in core
- (ii) friction loss
- (iii) windage loss
- (iv) armature cu-loss

$$(I_0 - I_{sh})^2 \times R_a$$

$I_{a0}^2 R_a$

If we subtract from total input no-load armature loss we get constant losses.

$$W_c = V I_0 - (I_0 - I_{sh})^2 R_a$$

for motor

$$\text{Input} = V I$$

$$\text{Armature Cu loss} = I_a^2 R_a = (I - I_{sh})^2 R_a$$

$$\text{const loss} = W_c$$

$$\eta_m = \frac{\text{input} - \text{total loss}}{\text{input}}$$

$$= \frac{V I - (I - I_{sh})^2 R_a - W_c}{V I}$$

for generator

$$\text{Output} = V I$$

$$\eta = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{V I}{V I + (I + I_{sh})^2 R_a + W_c}$$

Advantages :-

→ It is economical because power required to test a large machine is small

→ Efficiency ~~can~~ can be predetermined at any load b/c const. losses are known

Disadvantages

## Disadvantages

- > Change in iron loss from no load to full-load is not considered.
- > As the test is on no-load it is impossible to know whether commutator would be satisfactory at full-load and whether temperature rise would be within the specified limits.

## Applications of DC motors

### Shunt

- > centrifugal pumps, machine tools, blowers, fans etc.

### Series

For traction, Trolley, cars, cranes, hoists etc.

### Cumulative compound

Elevators, conveyors, Rolling mills, printing press, Air compressors etc.