

4TH SEM./ELECTRICAL./EEE/EE(INST. & CON.)/ 2024(S)

TH-2 Analog Electronics and OPAMP

Full Marks: 80

Time- 3 Hrs

Answer any five Questions including Q No.1& 2
Figures in the right-hand margin indicates marks

1. Answer **All** questions 2 x 10
 - a. Define Zener and Avalanche break down voltage.
 - b. Mention the advantages of negative feedback.
 - c. State Barkhausen criterion for sustained oscillation.
 - d. Why FET is called unipolar device and BJT is called bipolar device?
 - e. Define stabilization and stability factor.
 - f. Draw the equivalent circuit of OP-AMP.
 - g. Why CE configuration is most popular in amplifier circuit?
 - h. List the characteristics of ideal OP-AMP.
 - i. Define and classify transistor biasing.
 - j. State the difference between voltage and power amplifier.
2. Answer **Any Six** Questions 6 x 5
 - a. With a neat sketch explain the working of inverting and non inverting OP-AMP.
 - b. State the function of filter circuit in rectifier? Explain the working of capacitor input filter.
 - c. Explain the working of bridge rectifier and calculate (i) RMS current and voltage (ii) Ripple factor, (iii) Efficiency.
 - d. Derive the relationship between the current amplification factor of transistor.
 - e. Discuss the working of Zener diode and explain V-I characteristics.
 - f. With neat diagram derive the of I_C and V_{CE} using voltage divider biasing method.
 - g. Define Oscillator and Explain the working of Wein bridge oscillator.
3. Describe all types of transistor configuration with input and output characteristics. 10
4. Explain the working of a integrator and differentiator and derive the expression for its output voltage. 10
5. Define DC drain resistance, AC drain resistance and trans-conductance of FET and explain the working of FET. 10
6. With neat diagram explain the working of a class B push pull amplifier with its frequency response curve. 10
7. What is clamping circuit? Explain the function of positive clamper and negative clamper. 10