

3<sup>RD</sup> SEM./ ELE & MECH/ ELE. AND ETC./ELECTRICAL /  
EE(I&C) /ELECTICAL[PT]. / 2022(W)

Th-2 Circuit and Network Theory


Full Marks: 80

Time- 3 Hrs

Answer any five Questions including Q No.1& 2  
Figures in the right hand margin indicates marks

1. Answer **All** questions 2 x 10

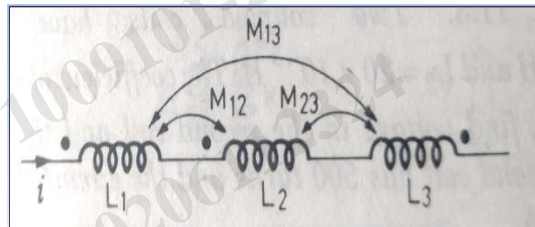- a. What is magnetizing force? Also state its SI unit.
- b. What do you mean by mesh analysis of AC networks?.
- c. State the Thevenin's theorem.
- d. Define (i) Q-factor (ii) Selectivity in series circuit
- e. Find the total inductance of three series connected coupled coils as shown below with  $L_1=1H$ ;  $L_2=2H$ ;  $L_3= 5H$ ,  
 $M_{12}=0.5H$ ;  $M_{23}=1H$ ;  $M_{13}=1H$




- f. Give an example of (i) Passive Element (ii) Non linear Element
- g. What do you mean by phase sequence in polyphase system?
- h. What is impedance and impedance triangle?
- i. Define filter. Give an example
- j. What are short-circuit admittance parameters?


2. Answer **Any Six** Questions 6 x 5

- a. Explain the hysteresis loop of magnetic materials in details with a neat diagram.
- b. How the 3-phase power is measured by two wattmeter method?
- c. Describe briefly about  $\pi$  section of a circuit network.

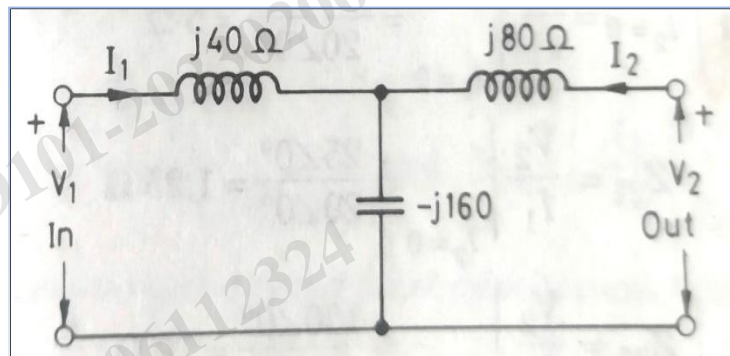- d. Write a short note on hybrid (h) parameters
- e. Find the open circuit parameters of the following two port network.



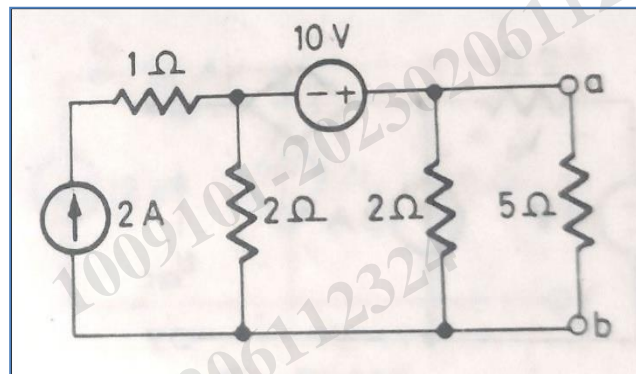- f. Explain the sinusoidal response of series R-C circuit.
- g. Find the current in  $5\Omega$  resistor using Norton's theorem across a-b terminals of the network shown below.



- |   |   |    |
|---|---|----|
| 3 | Derive the relation between phase and line quantities in star connection.             | 10 |
| 4 | Write short notes on (i) Source Transformation technique (ii) Dot Convention.         | 10 |
| 5 | Explain the transient response of series R-L-C circuit having DC Excitation.          | 10 |
| 6 | Write short notes on (i) Constant K low pass filter (ii) Star to delta transformation | 10 |
| 7 | Explain the series and parallel magnetic circuits in details with neat diagrams.      | 10 |